

# Chapter Two

---

## "Mathematical Models of Systems"

### 2.1 Definitions

Linear time invariant systems (LTIS)

it is represented by differential equation  
whose coefficients are constants.

for example:-

$$\frac{d^2x}{dt^2} + \frac{dx}{dt} + x = 0$$

$$\frac{d^2x}{dt^2} + \frac{dx}{dt} + x = A \sin wt$$

Transfer Function :- The transfer function of a linear, time-invariant differential equation system is defined as the ratio of Laplace transform of the output (response function)

to the Laplace transform of the input  
 (driving function) under the assumption  
 that all initial conditions are zero.

Consider the linear time-invariant system

$$a_0 \overset{(n)}{y} + a_1 \overset{(n-1)}{y} + \dots + a_{n-1} \overset{(1)}{y} + a_n y \\ = b_0 \overset{(m)}{x} + b_1 \overset{(m-1)}{x} + \dots + b_{m-1} \overset{(1)}{x} + b_m x$$

where :-

$$n \geq m$$

$y$ : is the output of system

$x$ : is the input of system.

Transfer function =  $G(s) = \frac{\underset{\text{Zero}}{\underset{|}{\mathcal{L}[\text{output}]}}}{\underset{\text{initial}}{\underset{|}{\mathcal{L}[\text{input}]}}} \Big|$

$$= \frac{Y(s)}{X(s)} = \frac{b_0 s^m + b_1 s^{m-1} + \dots + b_{m-1} s + b_m}{a_0 s^n + a_1 s^{n-1} + \dots + a_{n-1} s + a_n}$$

## 2.2. Modeling of Electrical System :-




Basic laws governing electrical circuits are Kirchhoff's current law and Voltage law.

- \* Kirchhoff's current law (node law) states that the algebraic sum of all currents entering and leaving anode is zero
- \* Kirchhoff's Voltage law (Loop law) states that at any given instant the algebraic sum of Voltages around any loop in an electrical circuit is zero.

A mathematical model of an electrical circuit can be obtained by applying one or both of Kirchhoff's Law to it.

The electrical system elements and their symbols are listed in table(2.1)

Table (2.1) Electrical system Elements

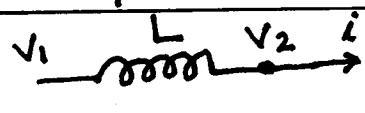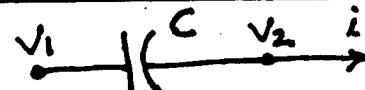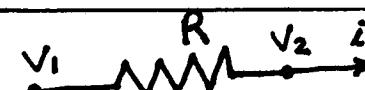Physical Element	Governing Equation	Symbol
Inductor	$V_{21} = L \frac{di}{dt}$	
Capacitor	$V_{21} = \frac{1}{C} \int i dt$	
Resistor	$V_{21} = RI$	

**ملخص** لد نے معادلاتے دریاختیار، یعنی تفود الدوائر  
لکھریاں ہی معادلاتے تفاصیلیہ میجب اسٹرنامِ حوَّلہ  
لد بدل سے لعڑھنے کا ماملہ مع ہذہ معادلاتے  
لذک یہ کہنے کتابتے علاقاتے المؤلیہ لکھ من، ملک، انسان  
و المقامہ کہا یا کے :-

$$V_R = i R \rightarrow V_R = I R$$


$$V_L = L \frac{di}{dt} \rightarrow V_L = L S I$$

$$V_C = \frac{1}{C} \int i dt \rightarrow V_C = \frac{1}{CS} I$$

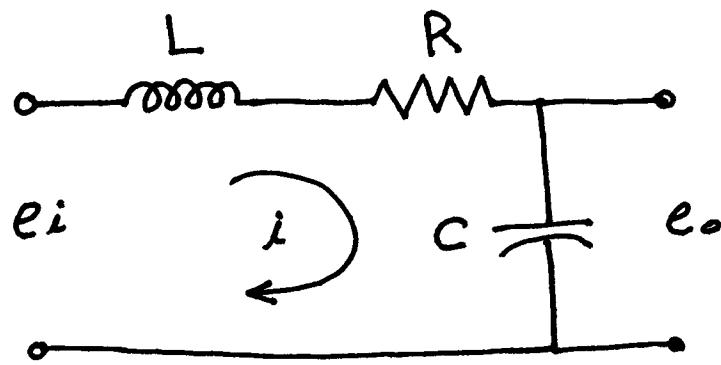Example :-

obtain the transfer function  $E_o(s)/E_i(s)$

for the electrical system shown in Fig below.



Solution :-

$$L \frac{di}{dt} + Ri + \frac{1}{C} \int i dt = E_i$$

$$\frac{1}{C} \int i dt = E_o$$


Taking the Laplace transform, assuming zero initial conditions, we obtain:-

$$L s I(s) + R I(s) + \frac{1}{C s} I(s) = E_i(s)$$

$$\frac{1}{C s} I(s) = E_o(s)$$

$$T.F. = \frac{E_o(s)}{E_i(s)} = \frac{1}{LC s^2 + RC s + 1}$$

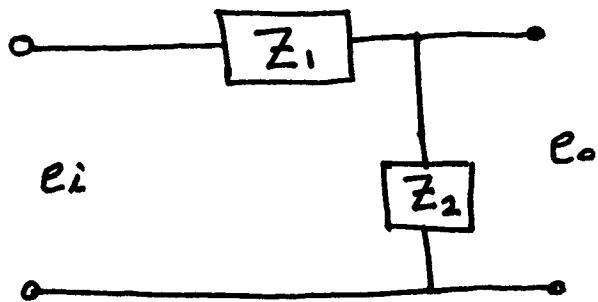another Solution for Example  
using complex impedance



$$Z_1 = Ls + R$$

$$Z_2 = \frac{1}{Cs}$$

$$E_i = RI(s) + Ls I(s) + \frac{1}{Cs} I(s)$$


$$E_o = \frac{1}{Cs} I(s)$$

$$\begin{aligned} \text{So } \frac{E_o(s)}{E_i(s)} &= \frac{\frac{1}{Cs}}{Ls + R + \frac{1}{Cs}} \times \frac{Cs}{Cs} \\ &= \frac{L}{Ls^2 + Rs + L} \end{aligned}$$
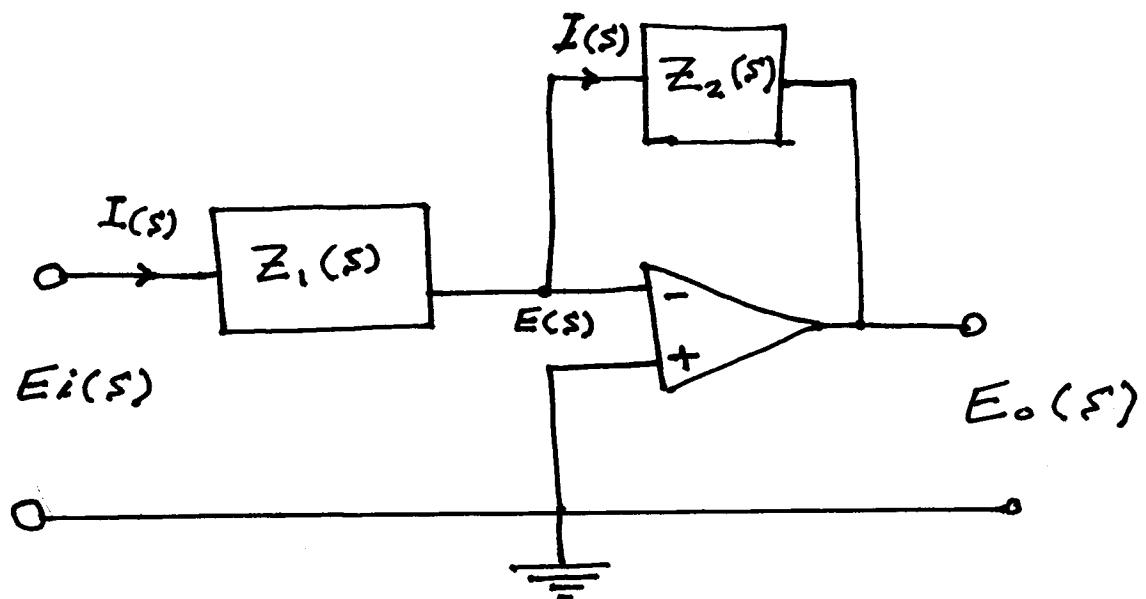
## 2.3. Modeling of electronic system

operational amplifier so

operational amplifier, often is called op-amps  
are frequently used to amplify signals.




operational amplifier circuit

$$\frac{E_o(s)}{E_i(s)} = -\frac{Z_2(s)}{Z_1(s)}$$

Example 80

obtain the transfer function  $E_o(s)/E_i(s)$  of the electronic system shown in the figure below

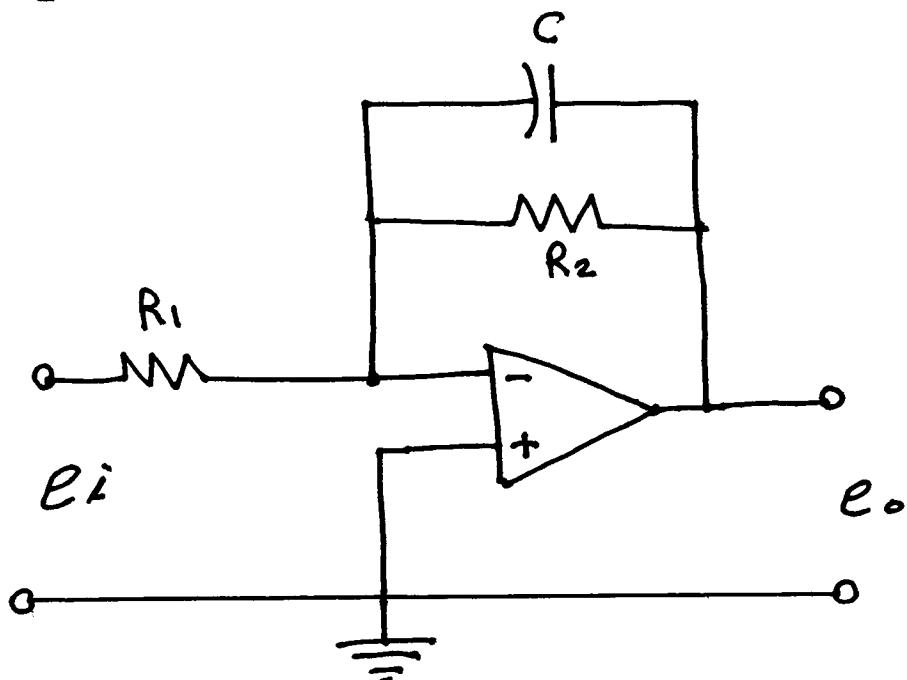

Solution 80

$$Z_1(s) = R_1 \quad \text{and} \quad Z_2(s) = \frac{1}{Cs + \frac{1}{R_2}} \\ = \frac{R_2}{R_2 Cs + 1}$$


The transfer function  $E_o(s)/E_i(s)$  is

$$T.F = \frac{E_o(s)}{E_i(s)} = \frac{-Z_2(s)}{Z_1(s)} = -\frac{R_2}{R_1} \frac{1}{R_2 Cs + 1}$$

مقدمة : هي حالة كون الدائرة الكهربائية تتكون من أُسْر

( Transfer function ) من دائرة فأن دالة الدستال

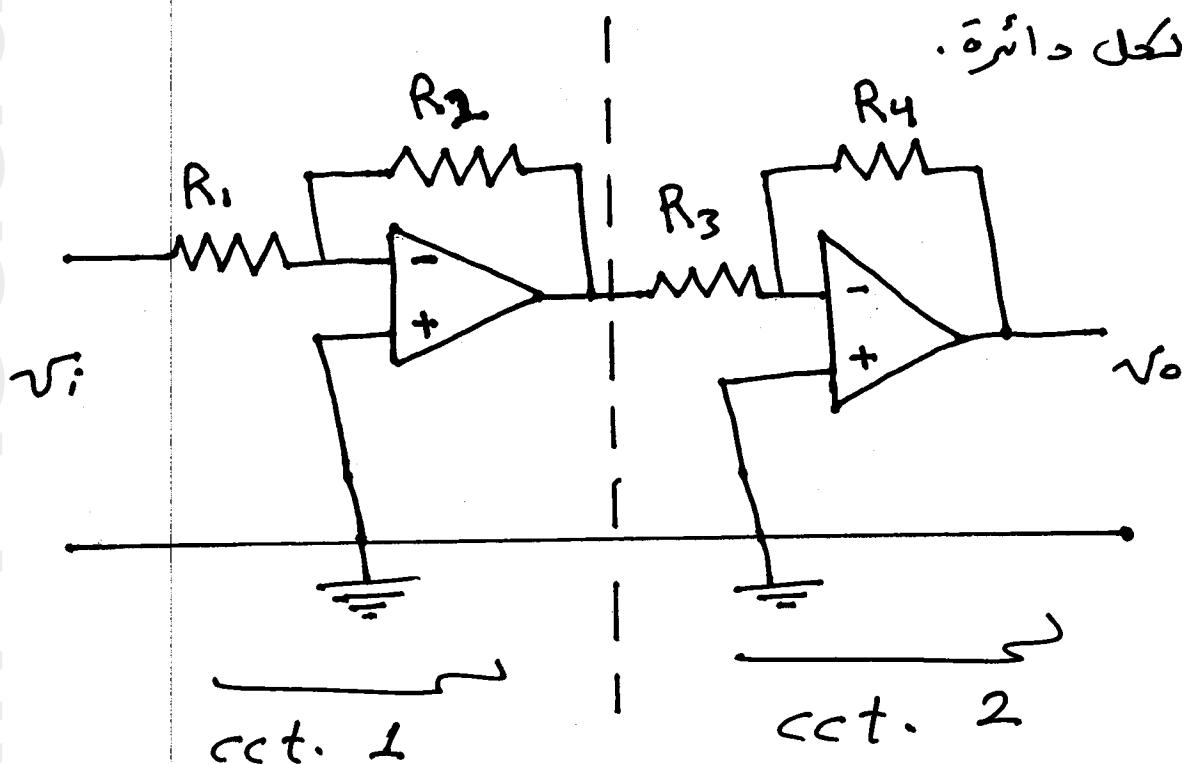ستكون حاصل ضرب دوال الدستال ( Transfer function )




لديجاد  $\frac{V_o}{V_i}$  نقوم بضرب دالة التحويل ( Transfer function ) للدائرة الدوكت بدالة التحويل ( Transfer function ) للدائرة

$$\frac{V_o}{V_i} = \left( -\frac{R_2}{R_1} \right) \times \left( \frac{-R_4}{R_3} \right) \text{ الناتج .}$$

$$= \frac{R_2 R_4}{R_1 R_3}$$

Example :-

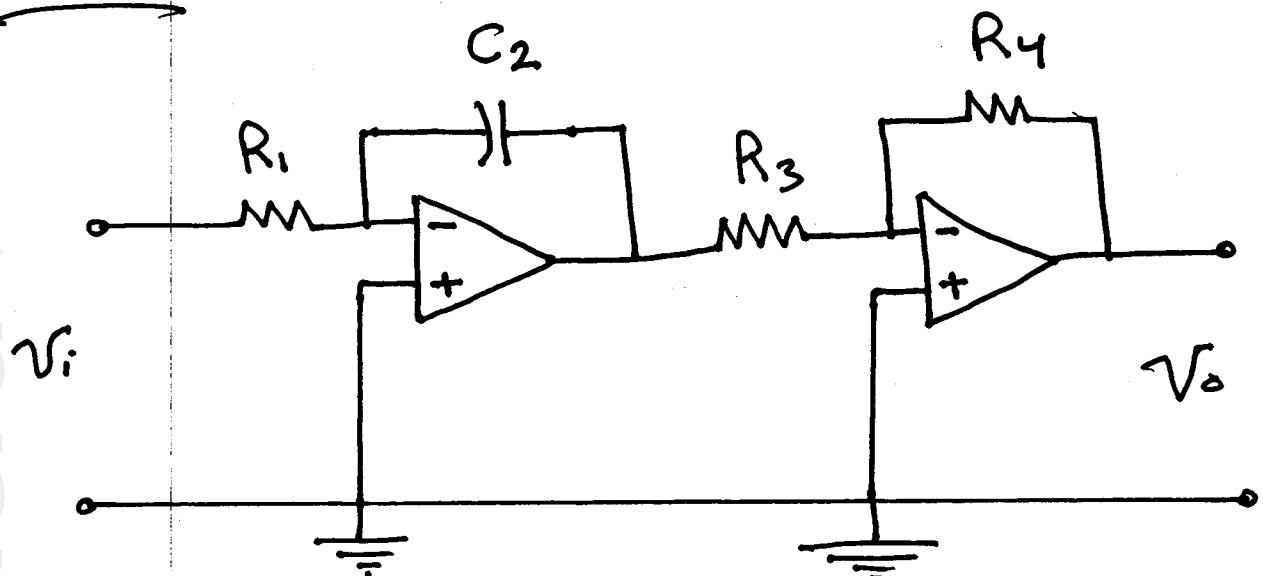

Find  $\frac{E_o(s)}{E_i(s)}$  Transfer function?

Solution :-

$$Z_1 = R_1$$

$$Z_3 = R_3$$

$$Z_2 = \frac{1}{C_2 s}$$


$$Z_4 = R_4$$

$$T.F. 1 = \frac{-Z_2}{Z_1}, \quad T.F. 2 = \frac{-Z_4}{Z_3}$$

$$T.F. \text{ total} = \frac{Z_2 Z_4}{Z_1 Z_3} = \frac{R_4}{R_3} \frac{1}{R_1 C_2 s}$$

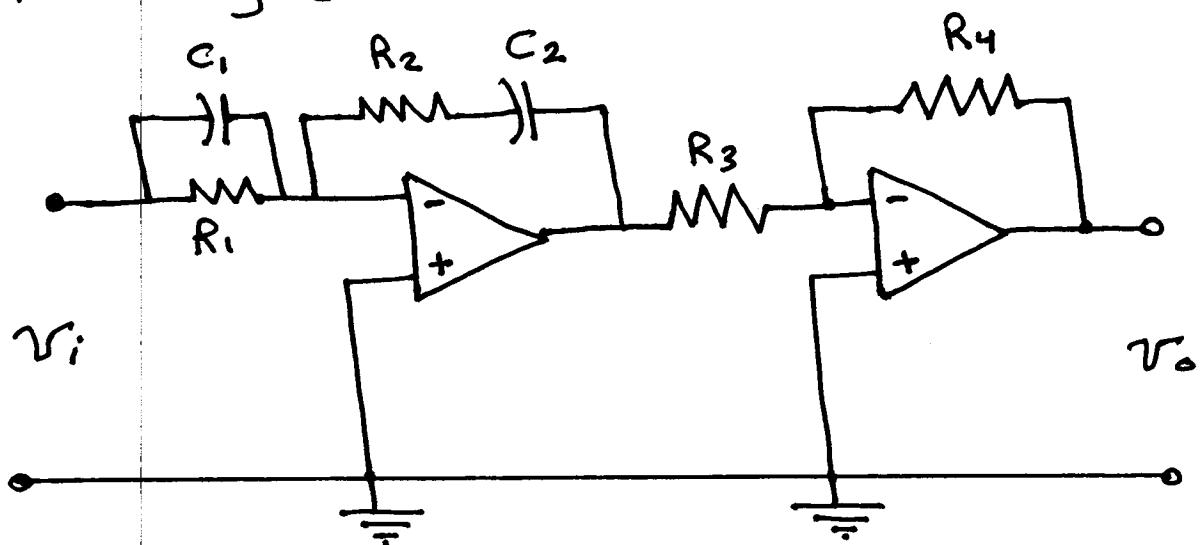Example ::

Find the transfer function for the following circuit




Solution ::

$$Z_1 = \frac{1}{C_1 s} \parallel R_1 = \frac{R_1}{R_1 C_1 s + 1}$$

$$Z_2 = R_2 + \frac{1}{C_2 s} = \frac{R_2 C_2 s + 1}{C_2 s}$$

$$Z_3 = R_3$$

$$Z_4 = R_4$$

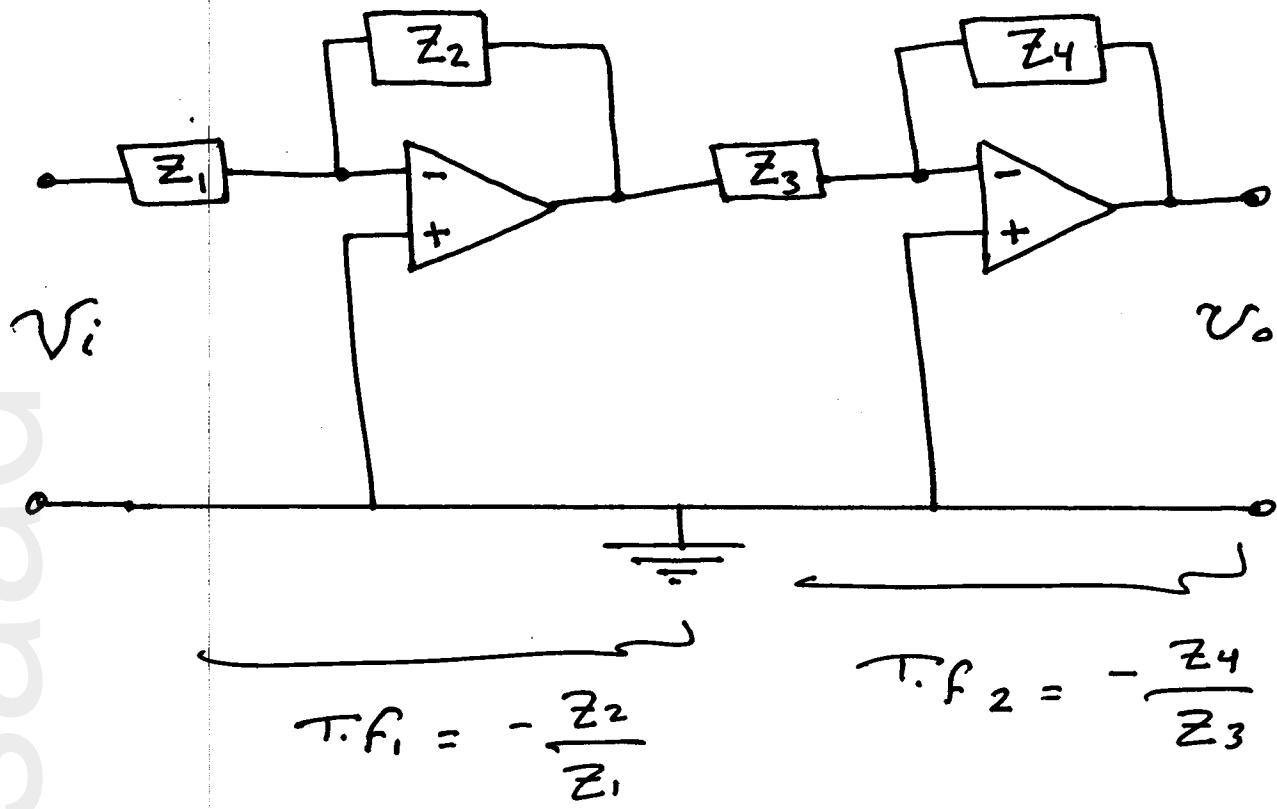

$$\begin{aligned}
 \text{Total T.F} &= \left( -\frac{Z_2}{Z_1} \right) \times \left( \frac{-Z_4}{Z_3} \right) \\
 &= \frac{Z_2 Z_4}{Z_1 Z_3}
 \end{aligned}$$

$$= \frac{\frac{R_2 C_2 s + 1}{C_2 s} \times R_4}{\frac{R_1}{R_1 C_1 s + 1} \times R_3}$$

$$= \frac{R_2 R_4}{R_1 R_3} \frac{(R_1 C_1 s + 1)(R_2 C_2 s + 1)}{R_2 C_2 s}$$