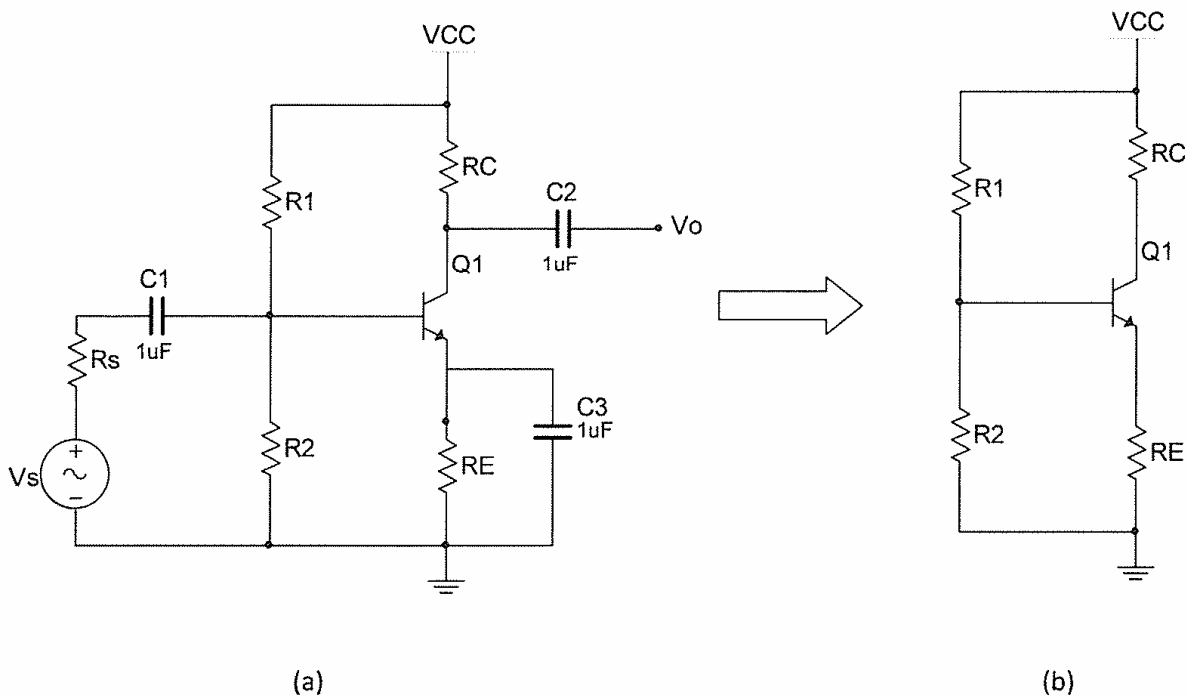


A.C Analysis of BJT Amplifiers

**For D.C analysis*

Open all the capacitors for example for the cct. Shown in Fig(1)



Fig(1) Transistor circuit under examination in D.C analysis

**for A.C analysis*

1. Setting all dc sources to zero and replacing them by a short-circuit equivalent
2. Replacing all capacitors by a short-circuit equivalent
3. Removing all elements bypassed by the short-circuit equivalents introduced by steps 1 and 2
4. Redrawing the network in a more convenient and logical form Fig(1a)

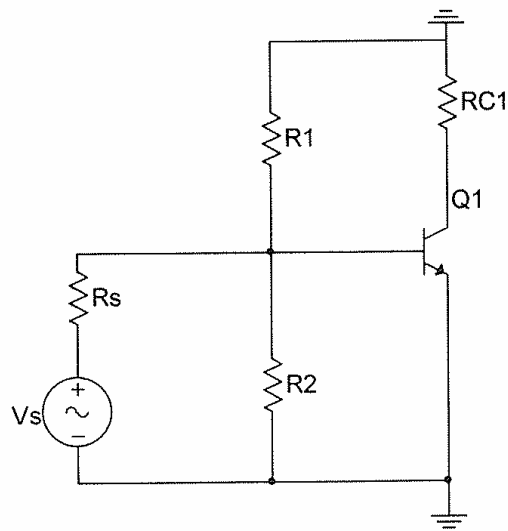


Figure (2) The network of Fig(1a) following removal of the dc supply and insertion of the short-circuit equivalent for the capacitors

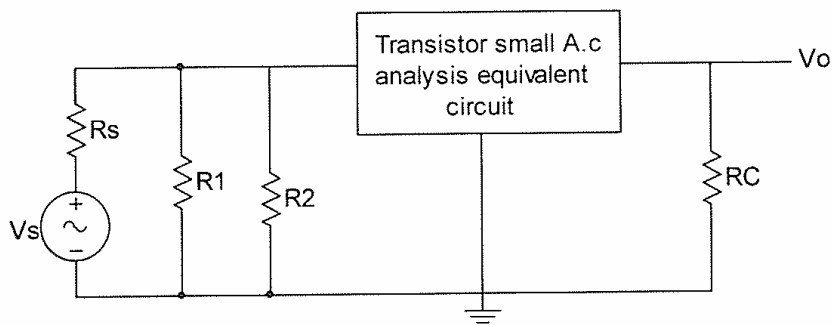


Figure 3 Circuit of Fig. 2 redrawn for small-signal ac analysis

BJT transistor modelling

1. The Hybrid Equivalent Model (Complete Model)

h_i = input resistor

h_r = reverse transfer voltage ratio

h_f = forward transfer current ratio

h_o = output conductance

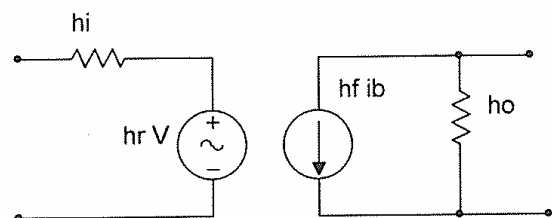


Fig.4 The Hybrid Equivalent Model

2. Approximate Equivalent Circuit

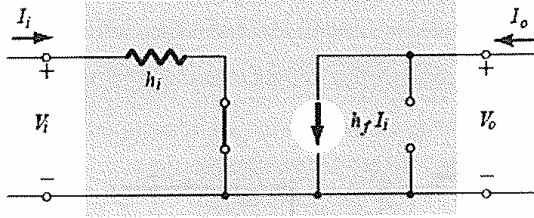


Figure 5a Effect of removing h_{re} and h_{oe} from the equivalent model

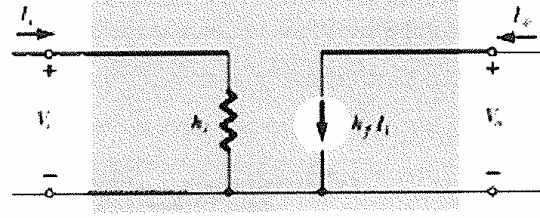


Figure 5b Approximate hybrid equivalent circuit.

3. The r_e Transistor Model

* Common base

$$r_e = \frac{26 \text{ mV}}{I_E}$$

$$Z_i = r_e \quad \text{CB}$$

$$Z_o \cong \infty \Omega \quad \text{CB}$$

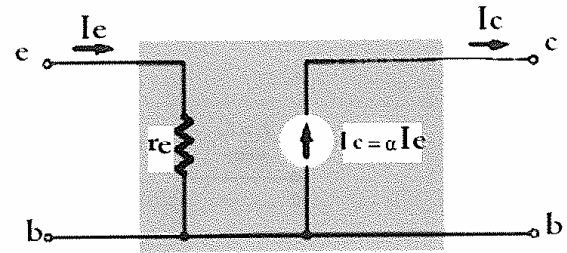


Fig.6 re-model 1

voltage gain will now be determined for the network of Fig. 2.14

$$V_o = -I_o R_L = -(-I_c) R_L = \alpha I_e R_L$$

$$V_i = I_e Z_i = I_e r_e$$

$$A_v = \frac{V_o}{V_i} = \frac{\alpha I_e R_L}{I_e r_e}$$

$$A_v = \frac{\alpha R_L}{r_e} \cong \frac{R_L}{r_e} \quad \text{CB}$$

$$A_i = \frac{I_o}{I_i} = \frac{-I_c}{I_e} = -\frac{\alpha I_e}{I_e}$$

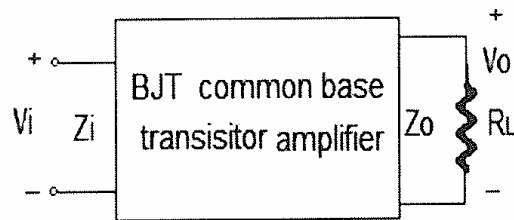


Figure 7 Defining A_v for the common-base configuration

$$A_i = -\alpha \cong -1 \quad \text{CB}$$

The approximation model for common base transistor shown in fig(2.15)

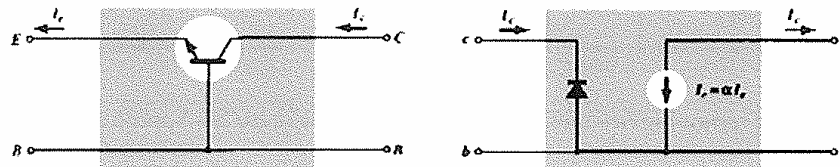


Figure 8 Approximate models for a common-base *npn* transistor configuration

*Common Emitter

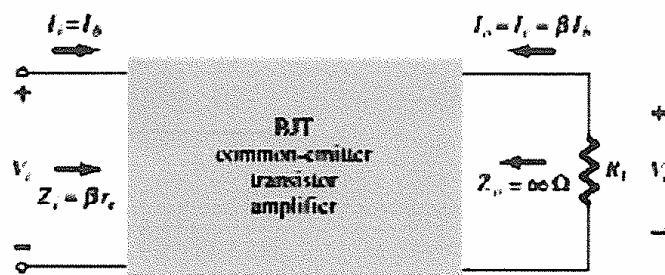


Figure 9 Determining the voltage and current gain for the common-emitter transistor amplifier.

$$V_o = -I_o R_L = -I_c R_L = -\beta I_b R_L$$

$$V_i = I_i Z_i = I_b \beta r_e$$

$$A_v = \frac{V_o}{V_i} = -\frac{\beta I_b R_L}{I_b \beta r_e}$$

$$A_v = -\frac{R_L}{r_e} \quad \text{CE, } r_o = \infty \Omega$$

The current gain for the configuration of Fig. 2.18

$$A_i = \frac{I_o}{I_i} = \frac{I_c}{I_b} = \frac{\beta I_b}{I_b}$$

$$A_i = \beta \quad CE, r_o = \infty \Omega$$

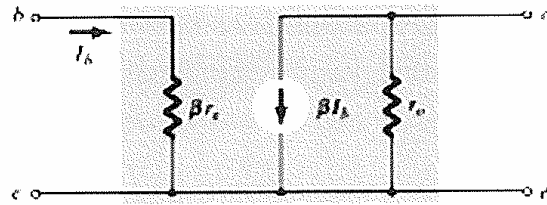


Figure 10 r_e model for the common-emitter transistor configuration

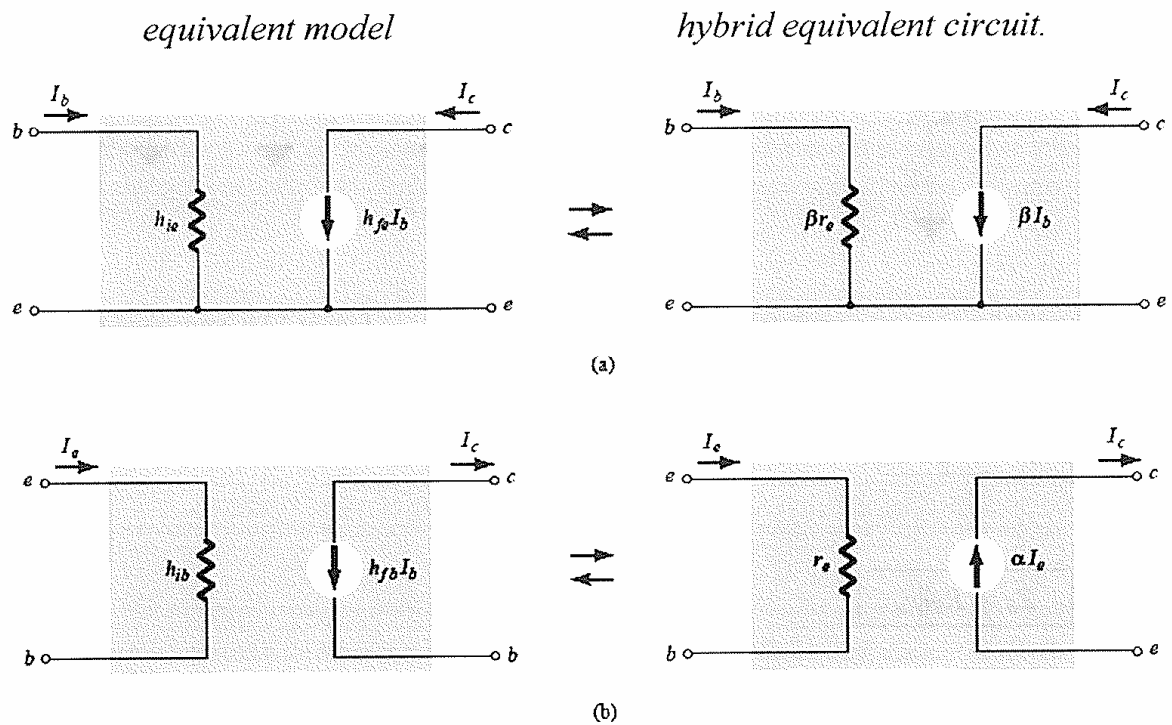


Figure 11 Hybrid versus r_e model: (a) common-emitter configuration;
(b) common-base configuration.

$$h_{ie} = \beta r_e, \quad h_{fe} = \beta$$

$$h_{ib} = r_e, \quad h_{fb} = -\alpha$$

BJT Small-Signal Analysis

1. Common-Emitter Amplifier Configuration

**Fixed-Bias*

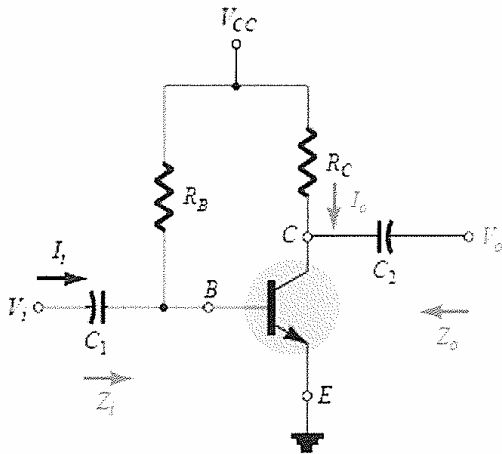


Figure 12.a Common-emitter fixed-bias

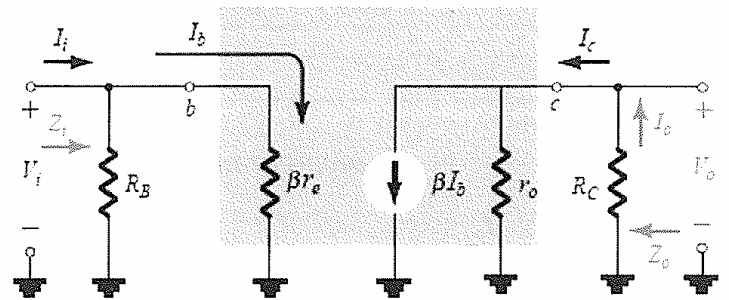


Figure 12.b equivalent circuit

$$Z_i = R_B \parallel \beta r_e$$

$$Z_o = R_C \parallel r_o$$

$$Z_o \cong R_C$$

If $r_o \geq 10 R_D$, the approximation $R_C \parallel r_o \cong R_C$ is frequently applied and

$$Z_i \cong \beta r_e$$

$$R_B \geq 10 \beta r_e$$

A_v : The resistors r_o and R_C are in parallel,

and

$$V_o = -\beta I_b (R_C \parallel r_o)$$

but

$$I_b = \frac{V_i}{\beta r_e}$$

so that

$$V_o = -\beta \left(\frac{V_i}{\beta r_e} \right) (R_C \parallel r_o)$$

and

$$A_v = \frac{V_o}{V_i} = -\frac{(R_C \parallel r_o)}{r_e}$$

If $r_o \geq 10R_C$,

$$A_v = -\frac{R_C}{r_e} \quad r_o \geq 10R_C$$

$$A_i = \frac{I_o}{I_i} = \frac{\beta R_B r_o}{(r_o + R_C)(R_B + \beta r_e)}$$

which is certainly an unwieldy, complex expression.

However, if $r_o \geq 10R_C$ and $R_B \geq 10\beta r_e$, which is often the case,

$$A_i = \frac{I_o}{I_i} \cong \frac{\beta R_B r_o}{(r_o)(R_B)}$$

and

$$A_i \cong \beta \quad r_o \geq 10R_C \quad R_B \geq 10\beta r_e$$

Phase Relationship: The negative sign in the resulting equation for A_v reveals that a 180° phase shift occurs between the input and output signals, as shown in Fig. 13.

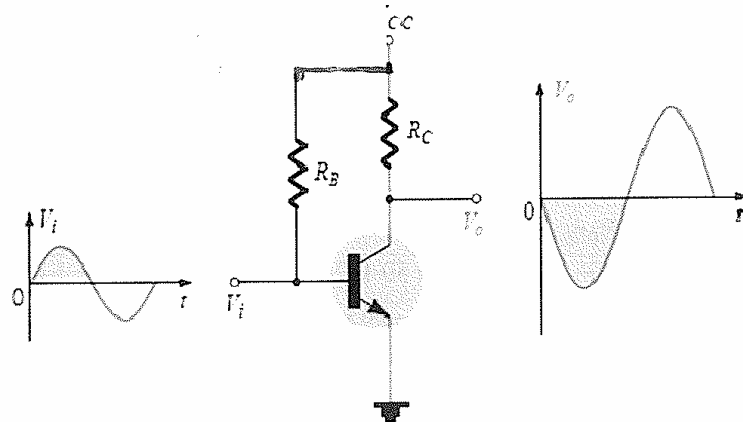


Figure (13) Demonstrating the 180° phase shift between inputs and output waveforms.

Example:1

For the network of Fig.(14):

- Determine r_e .
- Find Z_i (with $r_o = \infty \Omega$).
- Calculate Z_o (with $r_o = \infty \Omega$).
- Determine A_v (with $r_o = \infty \Omega$).
- Find A_i (with $r_o = \infty \Omega$).
- Repeat parts (c) through (e) including $r_o = 50 \text{ k}\Omega$ in all calculations and compare results.

Solution

- (a) DC analysis:

$$I_B = \frac{V_{CC} - V_{BE}}{R_B} = \frac{12 \text{ V} - 0.7 \text{ V}}{470 \text{ k}\Omega} = 24.04 \mu\text{A}$$

$$I_E = (\beta + 1)I_B = (101)(24.04 \mu\text{A}) = 2.428 \text{ mA}$$

$$r_e = \frac{26 \text{ mV}}{I_E} = \frac{26 \text{ mV}}{2.428 \text{ mA}} = 10.71 \Omega$$

- (b) $\beta r_e = (100)(10.71 \Omega) = 1.071 \text{ k}\Omega$

$$Z_i = R_B \parallel \beta r_e = 470 \text{ k}\Omega \parallel 1.071 \text{ k}\Omega = 1.069 \text{ k}\Omega$$

- (c) $Z_o = R_C = 3 \text{ k}\Omega$

$$(d) A_v = -\frac{R_C}{r_e} = -\frac{3 \text{ k}\Omega}{10.71 \Omega} = -280.11$$

- (e) Since $R_B \geq 10\beta r_e$ ($470 \text{ k}\Omega > 10.71 \text{ k}\Omega$)

$$A_i \cong \beta = 100$$

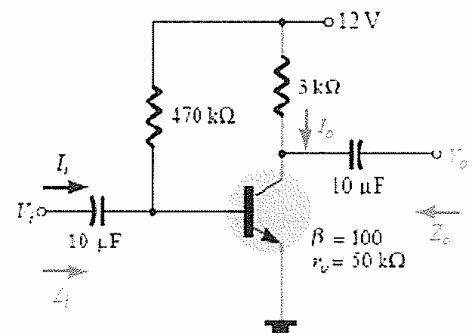


Figure 14.

- (f) $Z_o = r_o \parallel R_C = 50 \text{ k}\Omega \parallel 3 \text{ k}\Omega$ vs. $3 \text{ k}\Omega$

$$A_v = -\frac{r_o \parallel R_C}{r_e} = \frac{2.83 \text{ k}\Omega}{10.71 \Omega} = -264.24 \text{ vs. } -280.11$$

$$A_i = \frac{\beta R_B r_o}{(r_o + R_C)(R_B + \beta r_e)} = \frac{(100)(470 \text{ k}\Omega)(50 \text{ k}\Omega)}{(50 \text{ k}\Omega + 3 \text{ k}\Omega)(470 \text{ k}\Omega + 1.071 \text{ k}\Omega)} = 94.13 \text{ vs. } 100$$

As a check:

$$A_i = -A_v \frac{Z_i}{R_C} = \frac{-(-264.24)(1.069 \text{ k}\Omega)}{3 \text{ k}\Omega} = 94.16$$

Example: 2

For the network of Fig. 15 determined:

(a) Z_i , (b) Z_o (c) A_v (d) A_i


$$(a) \quad Z_i = R_B \parallel h_{ie} = 330 \text{ k}\Omega \parallel 1.175 \text{ k}\Omega \\ \cong h_{ie} = 1.171 \text{ k}\Omega$$

$$(b) \quad r_o = \frac{1}{h_{oe}} = \frac{1}{20 \text{ }\mu\text{A/V}} = 50 \text{ k}\Omega$$

$$Z_o = \frac{1}{h_{oe}} \parallel R_C = 50 \text{ k}\Omega \parallel 2.7 \text{ k}\Omega = 2.56 \text{ k}\Omega \cong R_C$$

$$(c) \quad A_v = -\frac{h_{fe}(R_C \parallel 1/h_{oe})}{h_{ie}} = -\frac{(120)(2.7 \text{ k}\Omega \parallel 50 \text{ k}\Omega)}{1.171 \text{ k}\Omega} =$$

$$(d) \quad A_i \cong h_{fe} = 120$$

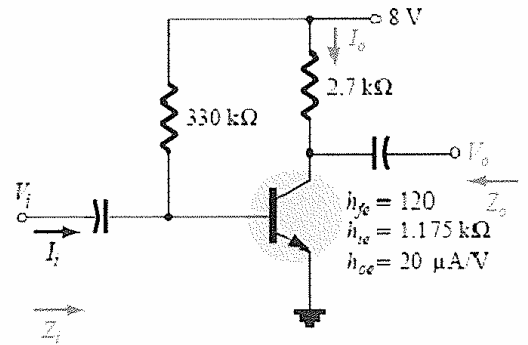

Fig(15)

*Voltage-divider

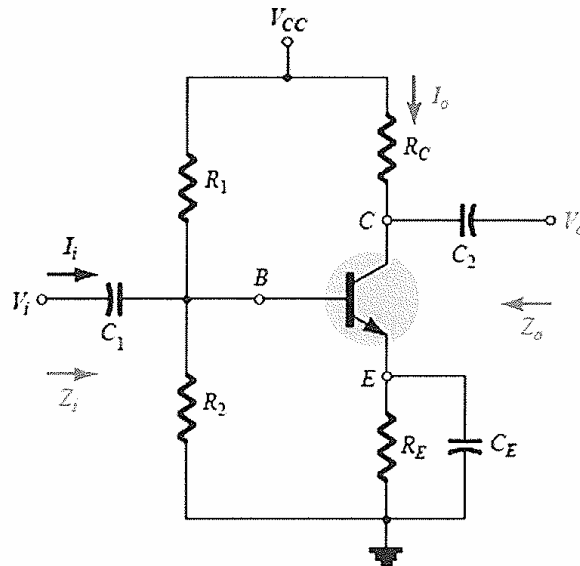


Figure 16.a Voltage-divider bias configurations.

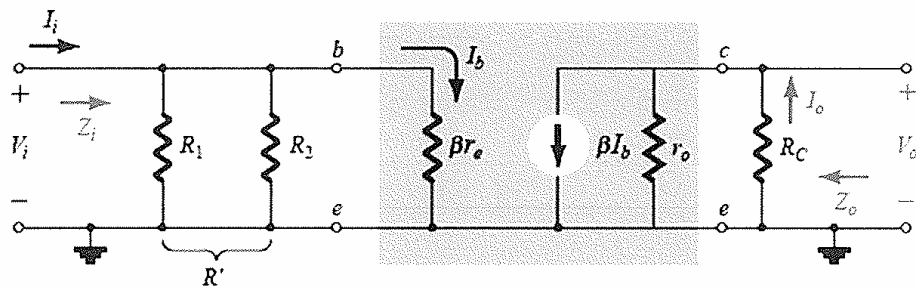


Figure 16.b Substituting the r_e equivalent circuit into the ac equivalent network of Fig. 16.a

$$R' = R_1 \parallel R_2 = \frac{R_1 R_2}{R_1 + R_2}$$

$$Z_i = R' \parallel \beta r_e$$

$$Z_o = R_C \parallel r_o$$

If $r_o \geq 10R_C$,

$$Z_o \cong R_C$$

$$A_v = \frac{V_o}{V_i} = \frac{-R_C \parallel r_o}{r_e}$$

For $r_o \geq 10R_C$,

$$A_v = \frac{V_o}{V_i} \cong -\frac{R_C}{r_e} \quad r_o \geq 10R_C$$

$$A_i = \frac{I_o}{I_i} = \frac{\beta R' r_o}{(r_o + R_C)(R' + \beta r_e)}$$

For $r_o \geq 10R_C$,

$$A_i = \frac{I_o}{I_i} \cong \frac{\beta R'}{R' + \beta r_e} \quad r_o \geq 10R_C$$

And if $R' \geq 10\beta r_e$,

$$A_i = \frac{I_o}{I_i} \cong \beta \quad r_o \geq 10R_C, R' \geq 10\beta r_e$$

$$A_i = -A_v \frac{Z_i}{R_C}$$

Phase relationship: The negative sign of equation above reveals a 180° phase shift between V_o and V_i .

Example : 3

For the network of Fig. 17, determine

- r_e .
- Z_i .
- Z_o ($r_o = \infty \Omega$).
- A_v ($r_o = \infty \Omega$).
- A_i ($r_o = \infty \Omega$).
- The parameters of parts (b) through (e) if $r_o = 1/h_{oe} = 50 \text{ k}\Omega$ and compare results.

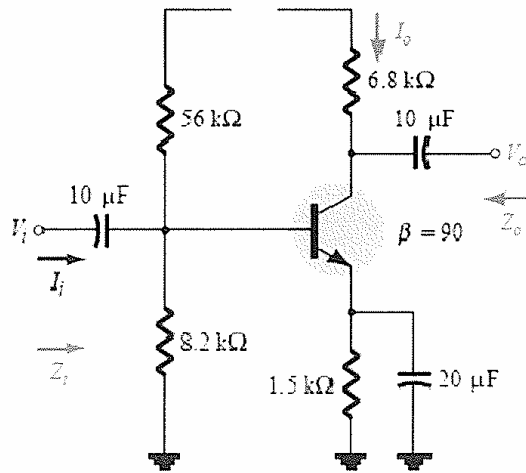


Figure 17 Example 3.

(a) DC: Testing $\beta R_E > 10R_2$

$$(90)(1.5 \text{ k}\Omega) > 10(8.2 \text{ k}\Omega)$$

$$135 \text{ k}\Omega > 82 \text{ k}\Omega \text{ (satisfied)}$$

Using the approximate approach,

$$V_B = \frac{R_2}{R_1 + R_2} V_{CC} = \frac{(8.2 \text{ k}\Omega)(22 \text{ V})}{56 \text{ k}\Omega + 8.2 \text{ k}\Omega} = 2.81 \text{ V}$$

$$V_E = V_B - V_{BE} = 2.81 \text{ V} - 0.7 \text{ V} = 2.11 \text{ V}$$

$$I_E = \frac{V_E}{R_E} = \frac{2.11 \text{ V}}{1.5 \text{ k}\Omega} = 1.41 \text{ mA}$$

$$r_e = \frac{26 \text{ mV}}{I_E} = \frac{26 \text{ mV}}{1.41 \text{ mA}} = 18.44 \text{ }\Omega$$

$$(b) R' = R_1 \parallel R_2 = (56 \text{ k}\Omega) \parallel (8.2 \text{ k}\Omega) = 7.15 \text{ k}\Omega$$

$$Z_i = R' \parallel \beta r_e = 7.15 \text{ k}\Omega \parallel (90)(18.44 \text{ }\Omega) = 7.15 \text{ k}\Omega \parallel 1.66 \text{ k}\Omega$$

$$= 1.35 \text{ k}\Omega$$

$$(c) Z_o = R_C = 6.8 \text{ k}\Omega$$

$$(d) A_v = -\frac{R_C}{r_e} = -\frac{6.8 \text{ k}\Omega}{18.44 \text{ }\Omega} = -368.76$$

(e) The condition $R' \geq 10\beta r_e$ ($7.15 \text{ k}\Omega \geq 10(1.66 \text{ k}\Omega) = 16.6 \text{ k}\Omega$) is *not* satisfied. Therefore,

$$A_i \cong \frac{\beta R'}{R' + \beta r_e} = \frac{(90)(7.15 \text{ k}\Omega)}{7.15 \text{ k}\Omega + 1.66 \text{ k}\Omega} = 73.04$$

(f) $Z_i = 1.35 \text{ k}\Omega$

$$Z_o = R_C \parallel r_o = 6.8 \text{ k}\Omega \parallel 50 \text{ k}\Omega = 5.98 \text{ k}\Omega \text{ vs. } 6.8 \text{ k}\Omega$$

$$A_v = -\frac{R_C \parallel r_o}{r_e} = -\frac{5.98 \text{ k}\Omega}{18.44 \Omega} = -324.3 \text{ vs. } -368.76$$

The condition

$$r_o \geq 10R_C \quad (50 \text{ k}\Omega \geq 10(6.8 \text{ k}\Omega) = 68 \text{ k}\Omega)$$

is *not* satisfied. Therefore,

$$\begin{aligned} A_i &= \frac{\beta R' r_o}{(r_o + R_C)(R' + \beta r_e)} = \frac{(90)(7.15 \text{ k}\Omega)(50 \text{ k}\Omega)}{(50 \text{ k}\Omega + 6.8 \text{ k}\Omega)(7.15 \text{ k}\Omega + 1.66 \text{ k}\Omega)} \\ &= 64.3 \text{ vs. } 73.04 \end{aligned}$$

There was a measurable difference in the results for Z_o , A_v , and A_i because the condition $r_o \geq 10R_C$ was *not* satisfied.

*Unbypassed configuration

$$V_i = I_b \beta r_e + I_e R_E$$

$$V_i = I_b \beta r_e + (\beta + 1)I_b R_E$$

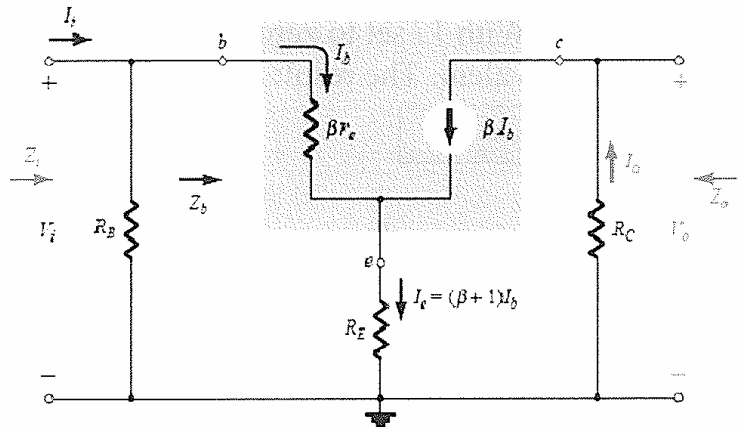
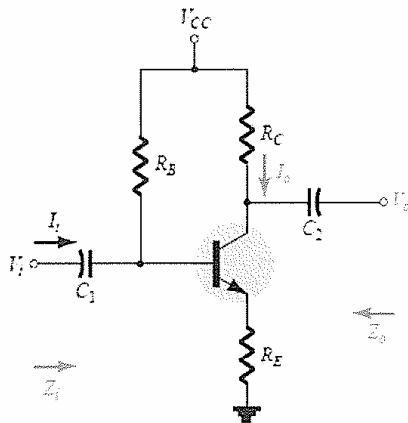


Figure 18.a CE emitter-bias configuration. Figure 18.b Substituting the r_e equivalent circuit

and the input impedance looking into the network to the right of R_B is

$$Z_b = \frac{V_i}{I_b} = \beta r_e + (\beta + 1)R_E$$

$$Z_b = \beta r_e + (\beta + 1)R_E$$

$$Z_b \cong \beta r_e + \beta R_E$$

$$Z_b \cong \beta(r_e + R_E)$$

$$Z_b \cong \beta(r_e + R_E)$$

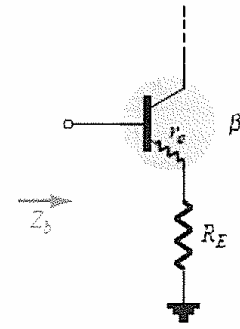


Figure 19 unbypassed emitter resistor.

Since R_E is often much greater than r_e , Eq. Above can be further reduced to

$$Z_b \cong \beta R_E$$

From fig 2.33 we can determined Z_i

$$Z_i = R_B || Z_b$$

Zo: With V_i set to zero, $I_B = 0$ and βI_B can be replaced by an open-circuit equivalent. The result is

$$Z_o = R_C$$

$$I_b = \frac{V_i}{Z_b}$$

$$V_o = -I_o R_C = -\beta I_b R_C$$

$$= -\beta \left(\frac{V_i}{Z_b} \right) R_C$$

$$A_v = \frac{V_o}{V_i} = -\frac{\beta R_C}{Z_b}$$

Substituting $Z_b = \beta(r_e + R_E)$ gives

$$A_v = \frac{V_o}{V_i} = -\frac{R_C}{r_e + R_E}$$

and for the approximation $Z_b \cong \beta R_E$,

$$A_v = \frac{V_o}{V_i} \cong -\frac{R_C}{R_E}$$

$$A_i = \frac{I_o}{I_i} = \frac{\beta R_B}{R_B + Z_b}$$

$$A_i = -A_v \frac{Z_i}{R_C}$$

Phase relationship: The negative sign in Equation above reveals a 180° phase shift between V_o and V_i .

2. Common-Base Amplifier Configuration

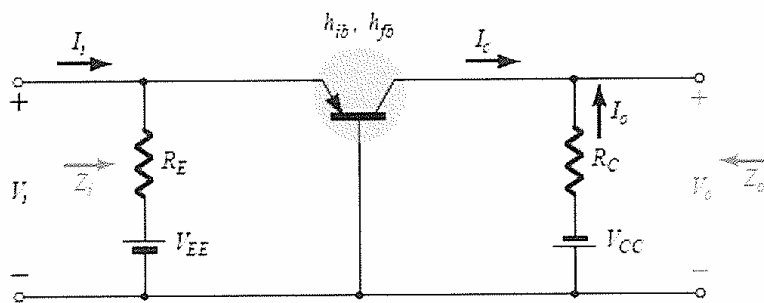


Figure 20.a Common-base configuration.

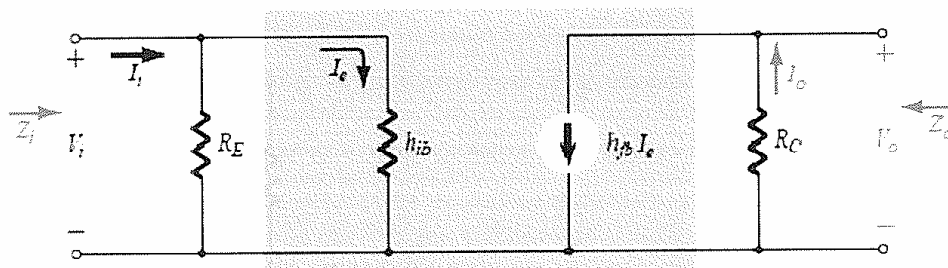


Figure 2.36 Substituting the approximate hybrid equivalent circuit into the ac equivalent network of Fig. 20.b

Example

For the network of Fig. 21, determine:

- (a) Z_i .
- (b) Z_o .
- (c) A_v .
- (d) A_i .

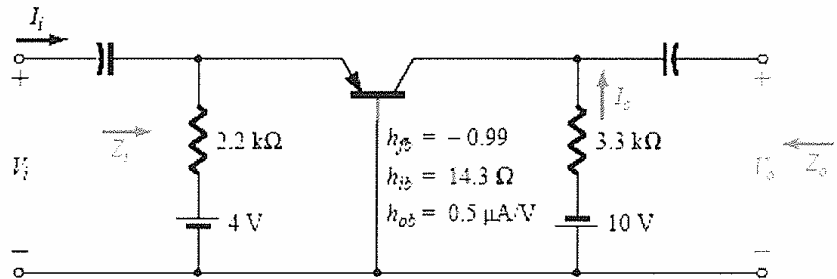


Fig.(21) Common base circuit

$$(a) Z_i = R_E \parallel h_{ib} = 2.2 \text{ k}\Omega \parallel 14.3 \text{ }\Omega = 14.21 \text{ }\Omega \cong h_{ib}$$

$$(b) r_o = \frac{1}{h_{ob}} = \frac{1}{0.5 \text{ }\mu\text{A/V}} = 2 \text{ M}\Omega$$

$$Z_o = \frac{1}{h_{ob}} \parallel R_C \cong R_C = 3.3 \text{ k}\Omega$$

$$(c) A_v = -\frac{h_{fb} R_C}{h_{ib}} = -\frac{(-0.99)(3.3 \text{ k}\Omega)}{14.21} = 229.91$$

$$(d) A_i \cong h_{fb} = -1$$

3. Common Collector Amplifier (Emitter Follower)

Main Characteristics of C.C.
Amplifier

- 1. $A_v < 1$
- 2. High R_i
- 3. Low R_o
- 4. Phase shift = zero

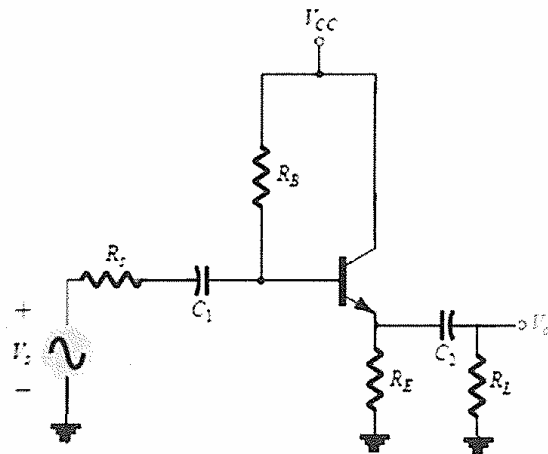


Fig.(22.a) Common collector circuit

Ac. Analysis of common collector with R_E

$$i_e = (1 + h_{fe})i_b$$

$$R_i = [(R_E \parallel R_L)(1 + h_{fe}) + h_{ie}] \parallel R_B$$

$$R_o = \left\{ \frac{[(R_s \parallel R_B) + h_{ie}]}{1 + h_{fe}} \right\} \parallel R_E$$

$$A_v = \frac{V_o}{V_i}$$

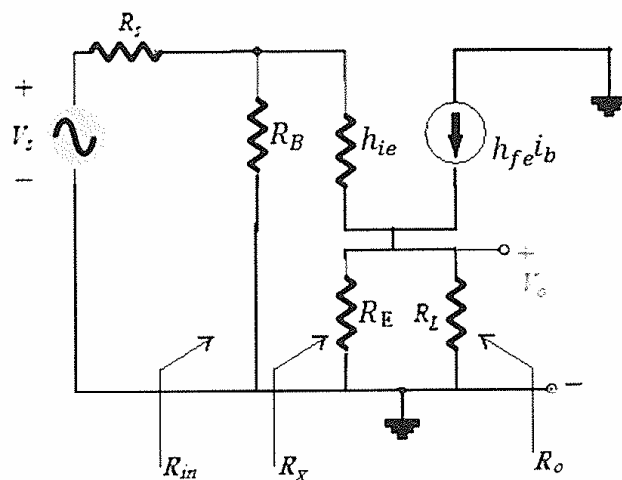


Fig.(22.b)

Equivalent circuit of common collector

$$A_v = \frac{i_b(1 + h_{fe})(R_E \parallel R_L)}{i_b[h_{ie} + (1 + h_{fe})(R_E \parallel R_L)]} \quad A_v < 1$$

$$A_{Is} = \frac{I_o}{I_i} = \frac{I_o}{I_b} * \frac{I_b}{I_i}$$

$$= \frac{(1 + h_{fe})R_E}{R_E + R_L} * \frac{R_B}{R_B + R_x}$$

$$R_x = h_{ie} + (1 + h_{fe})(R_E \parallel R_L)$$

H.w For the network of Fig. (23) $r_e = 28\Omega$ and $\beta = 200$

- Determine Z_i and Z_o .
- Find A_v and A_i .
- Draw V_o with input voltage $V_i = 100 \sin(\omega t)$. mV


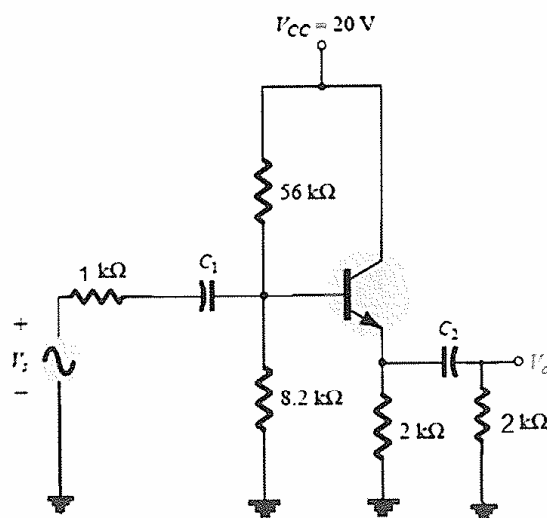


Fig. (23)


Field Effect Transistor (FET)

Main Characteristics

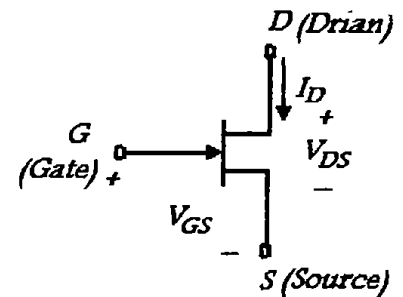- It is unipolar device
- It has a very high input impedance
- It is a voltage controlled current source (VCCS)
- Small size and widely used in I.C fabrication
- Low noise
- Low voltage gain



Fig(1) FET

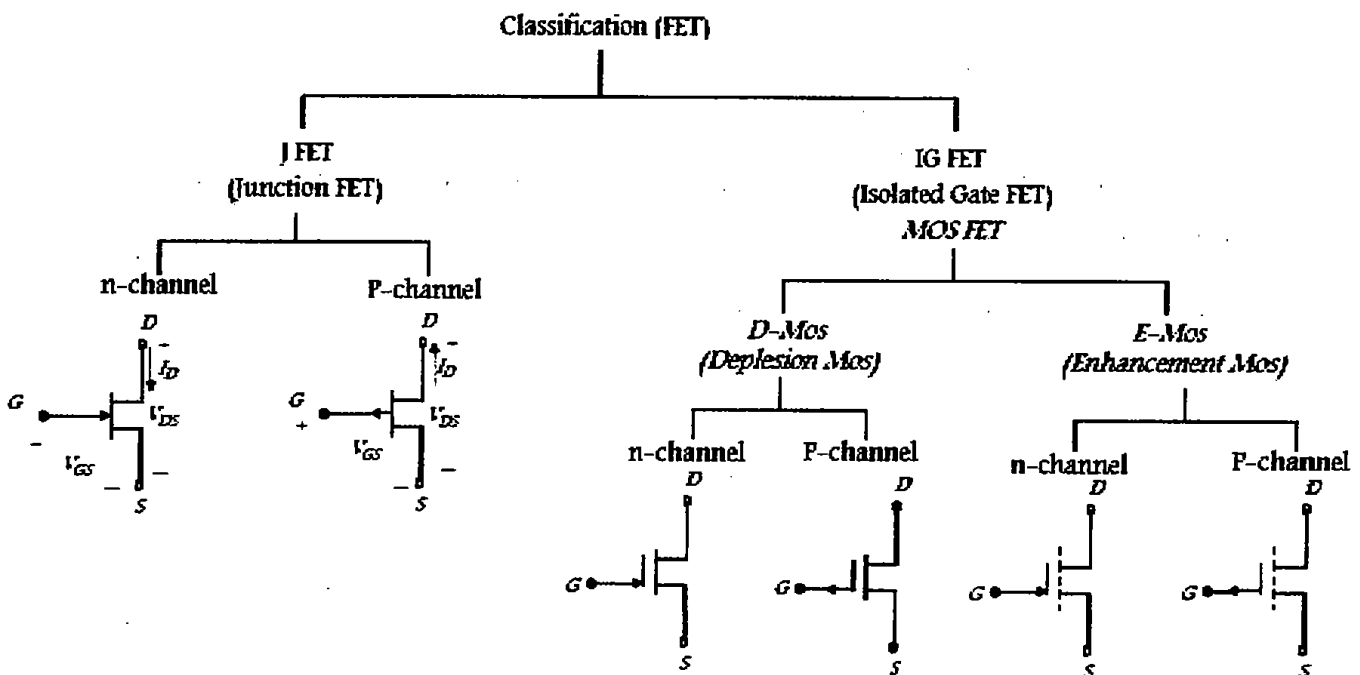


The main different between JFET & MOSFET are:


1. The MOSFET has an isolated liar between gate and drian and source therefore it has a very high input resistance compared to JFET
2. The MOSFET is very sensitive and effected by the static charge compared to the JFET which is rigid

Characteristics of JFET

Drain C/Cs (output C/Cs)

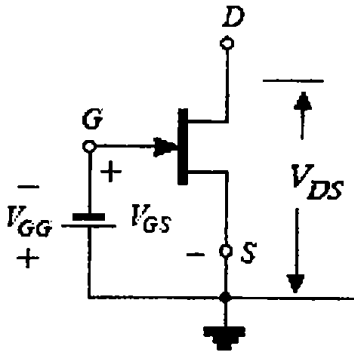

Fig(2a) JFET circuit

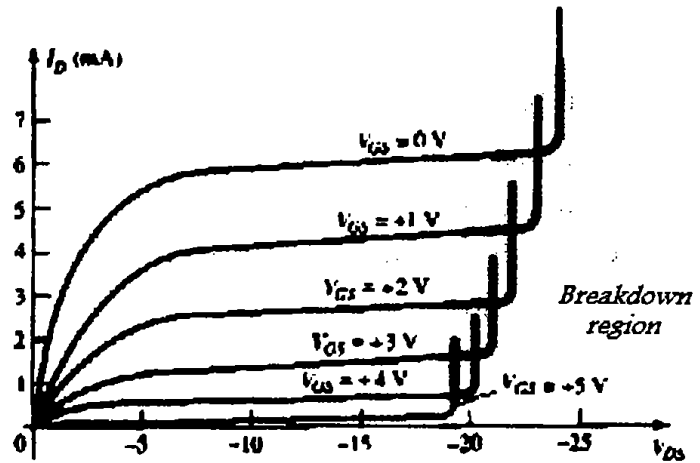


Fig(2b)c/cs of JFET

I_{DSS} = Drain source saturation current

V_p = Pinch-off voltage is negative voltage for n-channel devices and a positive voltage for p-channel JFETs

For active region operation G-S and D-S Jun must be reverse

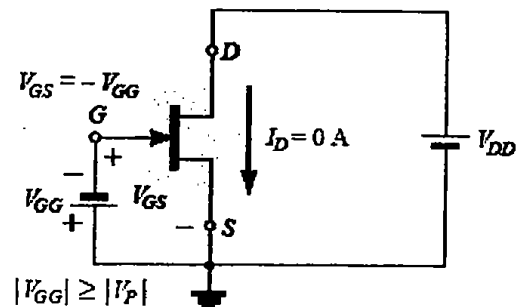$I_D = F(V_{GS})$ for a certian values of V_{GS}



Fig(3)


Transfer C/Cs

$I_D = F(V_{GS})$ and is given by Shockley's equation which is define by:

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_p} \right)^2$$

control variable

constants

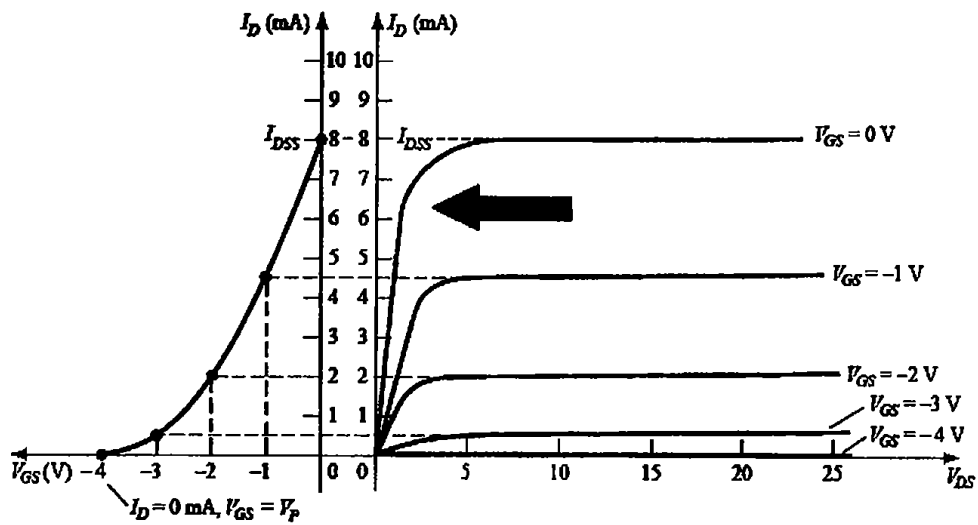

Fig(4) The transfer C/Cs of JFET


The transfer C/Cs can be draw when I_{DSS} and V_P are given

$V_{GS}(V)$	$I_D(mA)$
0	I_{DSS}
V_P	0
$\frac{1}{2}V_P$	$\frac{1}{4}I_{DSS}$
$\frac{1}{3}V_P$	$\frac{1}{2}I_{DSS}$

Example

Sketch the transfer curve for a p -channel device with $I_{DSS} = 4 \text{ mA}$ and $V_P = 3 \text{ V}$.


$V_{GS}(V)$	0	3	1.5	1
$I_D(mA)$	4	0	1	2

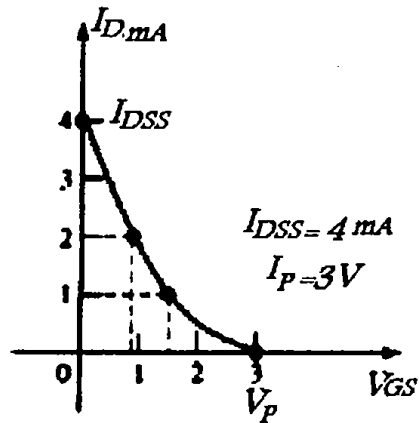


Fig(5) The transfer C/Cs

FET Biasing

- *FIXED-BIAS CONFIGURATION*

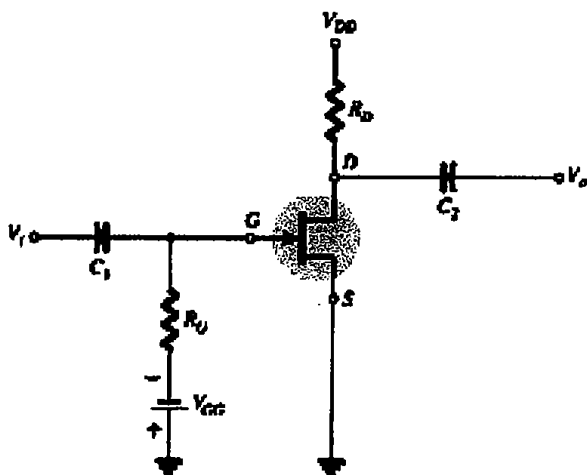

Fig(6a) Fixed bias of JFET

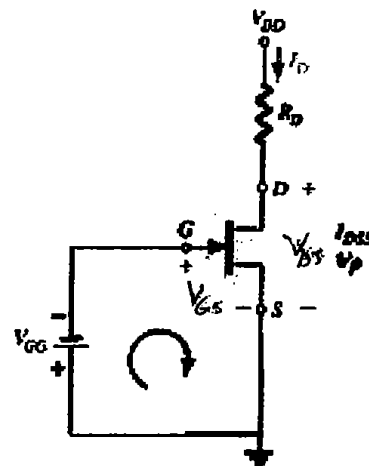

Fig(6b) dc analysis of JFET

$$V_{GS} = -V_{GG} \quad , \quad I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

The drain-to-source voltage of the output section can be determined by applying Kirchhoff's voltage law as follows:

$$+V_{DS} + I_D R_D - V_{DD} = 0$$

$$V_{DS} = V_{DD} - I_D R_D$$

$$V_S = 0 \text{ V}$$

$$V_{DS} = V_D - V_S$$

$$V_D = V_{DS} + V_S = V_{DS} + 0 \text{ V}$$

$$V_D = V_{DS}$$

$$V_{GS} = V_G - V_S$$

$$V_G = V_{GS} + V_S = V_{GS} + 0 \text{ V}$$


$$V_G = V_{GS}$$

Example

Determine the following for the network of fig (7)

(a) V_{GSQ} (b) I_{DQ} (c) V_{DS}

(d) V_D (e) V_G (f) V_S

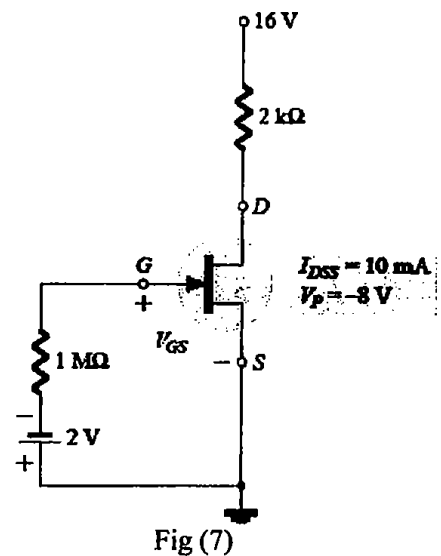

Mathematical Approach:

(a) $V_{GSQ} = -V_{GG} = -2 \text{ V}$

(b) $I_{DQ} = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2 = 10 \text{ mA} \left(1 - \frac{-2 \text{ V}}{-8 \text{ V}} \right)^2$
 $= 10 \text{ mA} (1 - 0.25)^2 = 10 \text{ mA} (0.75)^2 = 10 \text{ mA} (0.5625)$
 $= 5.625 \text{ mA}$


(c) $V_{DS} = V_{DD} - I_D R_D = 16 \text{ V} - (5.625 \text{ mA})(2 \text{ k}\Omega)$
 $= 16 \text{ V} - 11.25 \text{ V} = 4.75 \text{ V}$

(d) $V_D = V_{DS} = 4.75 \text{ V}$

(e) $V_G = V_{GS} = -2 \text{ V}$

(f) $V_S = 0 \text{ V}$

Graphical Approach

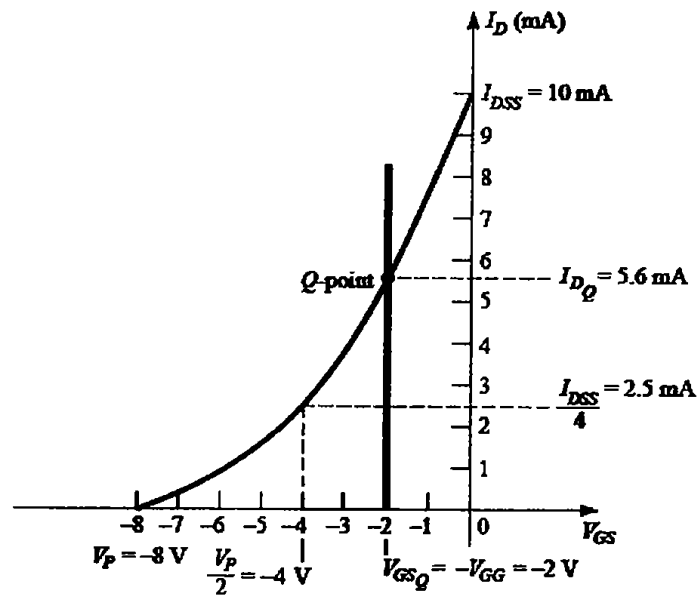

Fig(8) Graphically solution

$$V_{GSQ} = -V_{GG} = -2 \text{ V}$$

- (b) $I_{DQ} = 5.6 \text{ mA}$
- (c) $V_{DS} = V_{DD} - I_D R_D = 16 \text{ V} - (5.6 \text{ mA})(2 \text{ k}\Omega)$
 $= 16 \text{ V} - 11.2 \text{ V} = 4.8 \text{ V}$
- (d) $V_D = V_{DS} = 4.8 \text{ V}$
- (e) $V_G = V_{GS} = -2 \text{ V}$
- (f) $V_S = 0 \text{ V}$

• SELF-BIAS CONFIGURATION

The controlling gate-to-source voltage is now determined by the voltage across a resistor R_S introduced in the source leg of the configuration

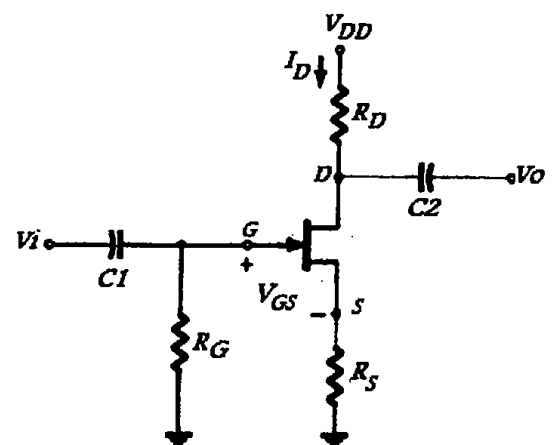


Fig (9) self bias

For the dc analysis, the capacitors can again be replaced by “open circuits

$$-V_{GS} - V_{R_s} = 0$$

$$V_{GS} = -V_{R_s}$$

$$V_{GS} = -I_D R_S$$

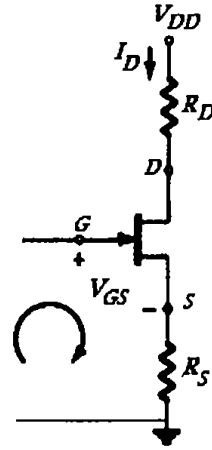


Fig (10) dc analysis of self bias

The level of V_{DS} can be determined by applying Kirchhoff's voltage law to the output circuit, with the result that

$$V_{R_s} + V_{DS} + V_{R_D} - V_{DD} = 0$$

$$V_{DS} = V_{DD} - V_{R_s} - V_{R_D} = V_{DD} - I_S R_S - I_D R_D$$

$$I_D = I_S$$

$$V_{DS} = V_{DD} - I_D(R_S + R_D)$$

$$V_S = I_D R_S$$

$$V_G = 0 \text{ V}$$

$$V_D = V_{DS} + V_S = V_{DD} - V_{R_D}$$

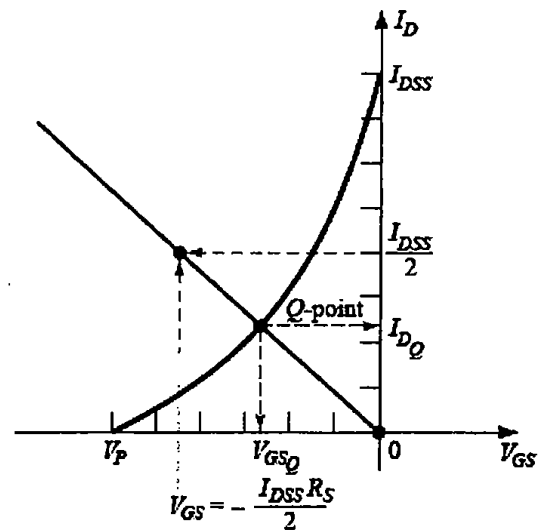


Fig (11) D.L.L


Example

Determine the following for the network of Fig.

(12)

(a) V_{GSQ} (b) I_{DQ} (c) V_{DS}

(d) V_S (e) V_G (f) V_D

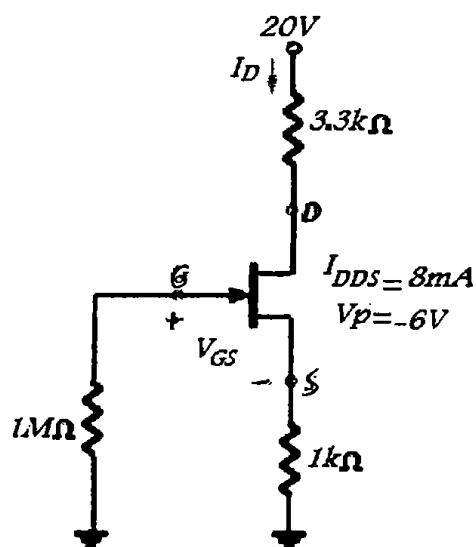

(a) The gate-to-source voltage is determined by

$$V_{GS} = -I_D R_S$$

Choosing $I_D = 4$ mA, we obtain

$$V_{GS} = -(4 \text{ mA})(1 \text{ k}\Omega) = -4 \text{ V}$$

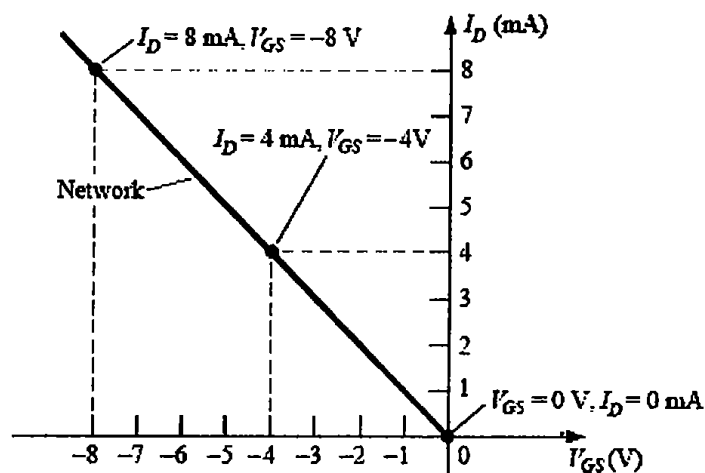


Figure 13 Sketching the selfbias line for the network of Fig12.

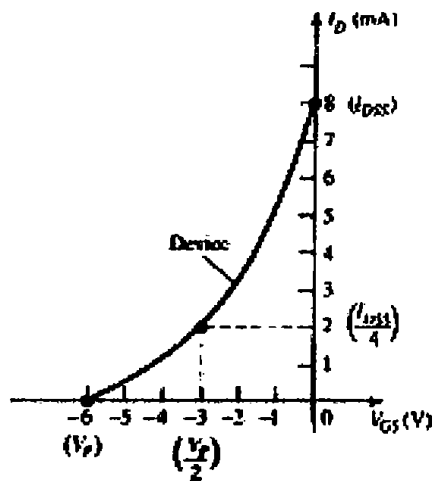


Figure.14 Sketching the device characteristics the for the JFET of Fig. 12.

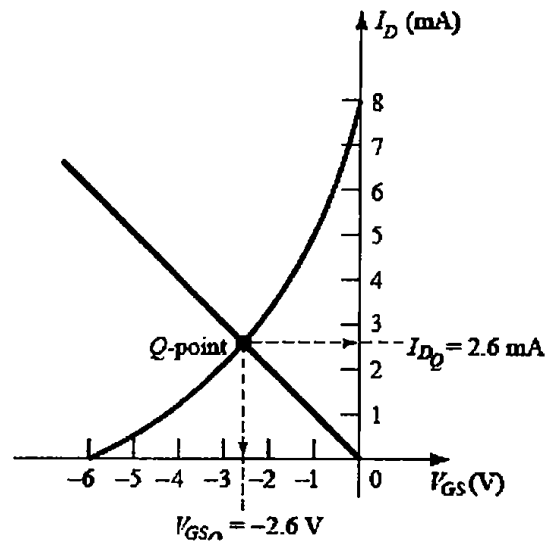


Figure 15 Determining the Q -point for network of Fig. 12.

(b) At the quiescent point:

$$I_{DQ} = 2.6 \text{ mA}$$

$$\begin{aligned} \text{(c)} \quad V_{DS} &= V_{DD} - I_D(R_S + R_D) \\ &= 20 \text{ V} - (2.6 \text{ mA})(1 \text{ k}\Omega + 3.3 \text{ k}\Omega) \\ &= 20 \text{ V} - 11.18 \text{ V} \\ &= 8.82 \text{ V} \end{aligned}$$

$$\begin{aligned} \text{(d)} \quad V_S &= I_D R_S \\ &= (2.6 \text{ mA})(1 \text{ k}\Omega) \\ &= 2.6 \text{ V} \end{aligned}$$

$$\text{(e)} \quad V_G = 0 \text{ V}$$

$$\text{(f)} \quad V_D = V_{DS} + V_S = 8.82 \text{ V} + 2.6 \text{ V} = 11.42 \text{ V}$$

$$\text{or} \quad V_D = V_{DD} - I_D R_D = 20 \text{ V} - (2.6 \text{ mA})(3.3 \text{ k}\Omega) = 11.42 \text{ V}$$

Voltage-Divider Biasing


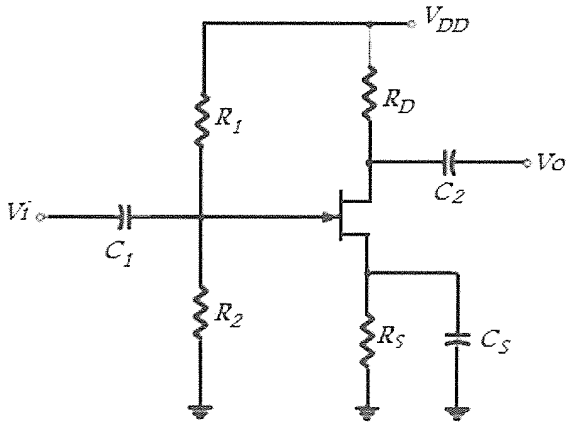


Fig (1a) Voltage divider bias arrangement

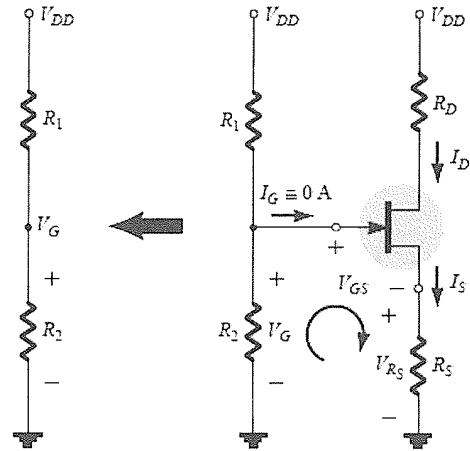

Redrawn network of fig (1b) for dc analysis

$$V_G = \frac{R_2 V_{DD}}{R_1 + R_2}$$

Applying Kirchhoff's voltage law in the clockwise direction to the indicated loop of Fig (1.b) will result in

$$V_G - V_{GS} - V_{RS} = 0$$

$$V_{GS} = V_G - V_{RS}$$

Substituting $V_{RS} = I_S R_S = I_D R_S$, we have


$$V_{GS} = V_G - I_D R_S$$

To draw c/cs

$$V_{GS} = V_G |_{I_D = 0 \text{ mA}}$$

$$V_{GS} = V_G - I_D R_S$$

$$0 \text{ V} = V_G - I_D R_S$$

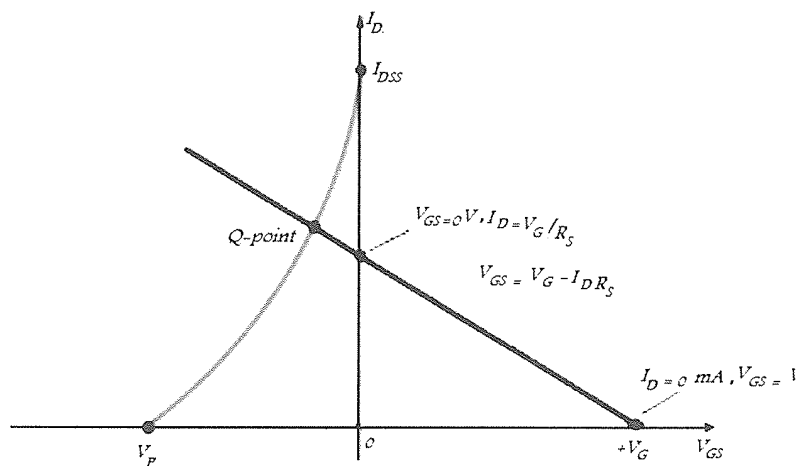

Fig(2) trans. c/cs

$$I_D = \frac{V_G}{R_S} \Big|_{V_{GS} = 0 \text{ V}}$$

$$V_{DS} = V_{DD} - I_D(R_D + R_S)$$

$$V_D = V_{DD} - I_D R_D$$

$$V_S = I_D R_S$$

$$I_{R_1} = I_{R_2} = \frac{V_{DD}}{R_1 + R_2}$$

Example

Determine the following for the network of Fig(3).

- (a) I_{DQ} and V_{GSQ} .
- (b) V_D .
- (c) V_S .
- (d) V_{DS} .
- (e) V_{DG} .

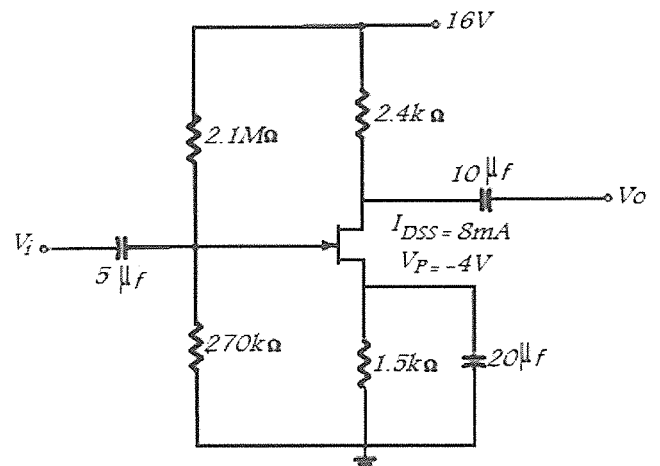



Fig (3) Voltage divider circuit

(a) for the transfer c/cs if $I_D = \frac{I_{DSS}}{4} =$

$$8\text{mA}/4 = 2\text{mA} ,$$

$$V_{GS} = \frac{V_P}{2} = -\frac{4\text{V}}{2} = -2$$

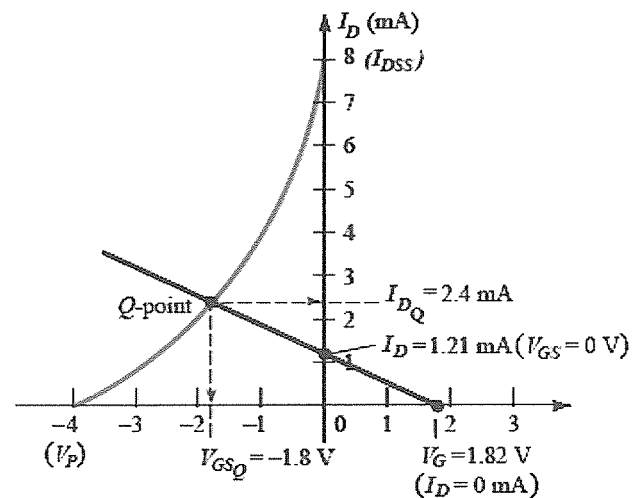The resulting curve representing Shockley's equation fig (4), then



Fig(4)

$$\begin{aligned}
V_G &= \frac{R_2 V_{DD}}{R_1 + R_2} \\
&= \frac{(270 \text{ k}\Omega)(16 \text{ V})}{2.1 \text{ M}\Omega + 0.27 \text{ M}\Omega} \\
&= 1.82 \text{ V}
\end{aligned}$$

$$\begin{aligned}
V_{GS} &= V_G - I_D R_S \\
&= 1.82 \text{ V} - I_D (1.5 \text{ k}\Omega)
\end{aligned}$$

When $I_D = 0 \text{ mA}$:

$$V_{GS} = +1.82 \text{ V}$$

When $V_{GS} = 0 \text{ V}$:

$$I_D = \frac{1.82 \text{ V}}{1.5 \text{ k}\Omega} = 1.21 \text{ mA}$$

The resulting bias line appears on Fig. 4 with quiescent values of

$$I_{DQ} = 2.4 \text{ mA}$$

$$V_{GSQ} = -1.8 \text{ V}$$

$$\begin{aligned}
\text{(b) } V_D &= V_{DD} - I_D R_D \\
&= 16 \text{ V} - (2.4 \text{ mA})(2.4 \text{ k}\Omega) \\
&= 10.24 \text{ V}
\end{aligned}$$

$$\begin{aligned}
\text{(c) } V_S &= I_D R_S = (2.4 \text{ mA})(1.5 \text{ k}\Omega) \\
&= 3.6 \text{ V}
\end{aligned}$$

$$\begin{aligned}
\text{(d) } V_{DS} &= V_{DD} - I_D (R_D + R_S) \\
&= 16 \text{ V} - (2.4 \text{ mA})(2.4 \text{ k}\Omega + 1.5 \text{ k}\Omega) \\
&= 6.64 \text{ V}
\end{aligned}$$

$$\begin{aligned}
\text{or } V_{DS} &= V_D - V_S = 10.24 \text{ V} - 3.6 \text{ V} \\
&= 6.64 \text{ V}
\end{aligned}$$

$$\begin{aligned}
V_{DG} &= V_D - V_G \\
&= 10.24 \text{ V} - 1.82 \text{ V} \\
&= 8.42 \text{ V}
\end{aligned}$$

Common Gate

Example

Determine the following for the common-gate configuration of Fig. 6.17.

- (a) V_{GSQ} .
- (b) I_{DQ} .
- (c) V_D .
- (d) V_G .
- (e) V_S .
- (f) V_{DS} .

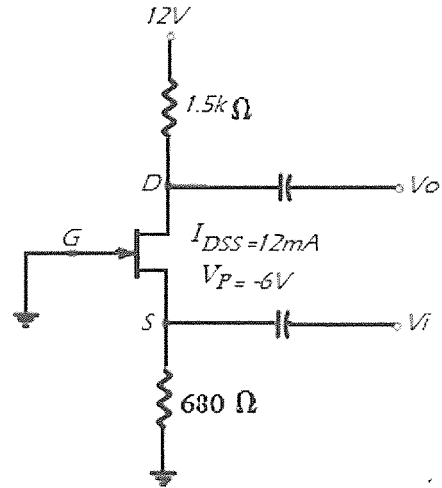


Fig (5a) Common gate circuit

- (a) The transfer characteristics and load line appear in Fig. 6.19. In this case, the second point for the sketch of the load line was determined by choosing (arbitrarily) $I_D = 6$ mA and solving for V_{GS} . That is,

$$V_{GS} = -I_D R_S = -(6 \text{ mA})(680 \Omega) = -4.08 \text{ V}$$

$$I_D = \frac{I_{DSS}}{4} = \frac{12 \text{ mA}}{4} = 3 \text{ mA} \quad , \quad V_{GS} = \frac{V_P}{2} = -\frac{6 \text{ V}}{2} = -3 \text{ V}$$

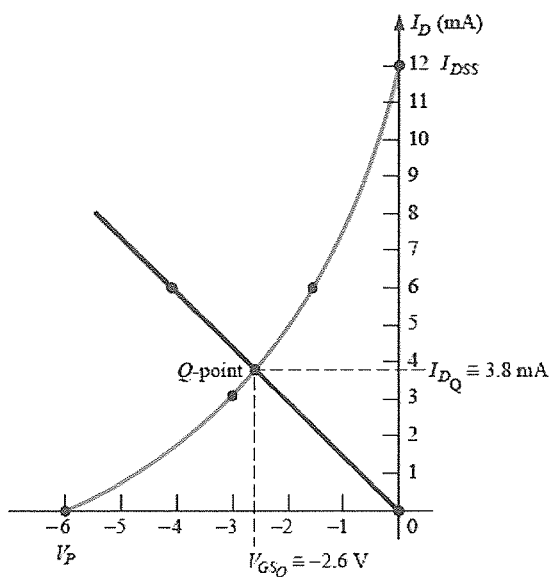


Figure 6 Determining the Q-point for the network of Fig.(5a)

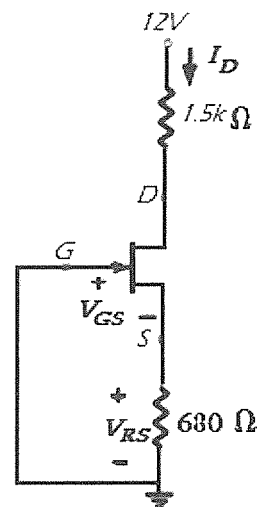


Figure (5b) Sketching the dc equivalent network of Fig. 5

as shown on Fig. 6 Using the resulting quiescent point of Fig. 6 results in

(b)

$$V_{GSQ} \cong -2.6 \text{ V}$$

$$I_{DQ} \cong 3.8 \text{ mA}$$

$$\begin{aligned} \text{(c)} \quad V_D &= V_{DD} - I_D R_D \\ &= 12 \text{ V} - (3.8 \text{ mA})(1.5 \text{ k}\Omega) = 12 \text{ V} - 5.7 \text{ V} \\ &= 6.3 \text{ V} \end{aligned}$$

$$\text{(d)} \quad V_G = 0 \text{ V}$$

$$\begin{aligned} \text{(e)} \quad V_S &= I_D R_S = (3.8 \text{ mA})(680 \text{ }\Omega) \\ &= 2.58 \text{ V} \end{aligned}$$

$$\begin{aligned} \text{(f)} \quad V_{DS} &= V_D - V_S \\ &= 6.3 \text{ V} - 2.58 \text{ V} \\ &= 3.72 \text{ V} \end{aligned}$$

Example

Determine the following for the network of fig (7a)


- (a) I_{DQ} and V_{GSQ} .
- (b) V_{DS} .
- (c) V_D .
- (d) V_S .

$$-V_{GS} - I_S R_S + V_{SS} = 0$$

$$V_{GS} = V_{SS} - I_S R_S$$

$$I_S = I_D$$

$$V_{GS} = V_{SS} - I_D R_S$$

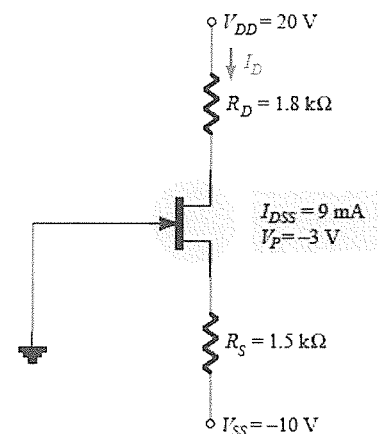

Fig(7a)

$$V_{GS} = 10 \text{ V} - I_D(1.5 \text{ k}\Omega)$$

For $I_D = 0 \text{ mA}$,


$$V_{GS} = V_{SS} = 10 \text{ V}$$

For $V_{GS} = 0 \text{ V}$,

$$0 = 10 \text{ V} - I_D(1.5 \text{ k}\Omega)$$

and
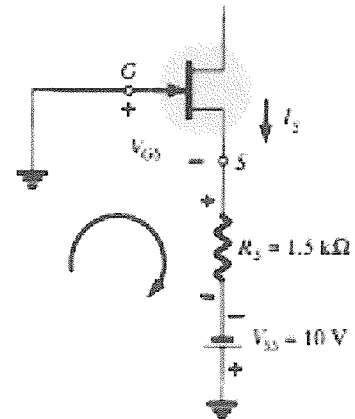
$$I_D = \frac{10 \text{ V}}{1.5 \text{ k}\Omega} = 6.67 \text{ mA}$$



Fig(7b) Determining the network equation for the configuration of Fig7a

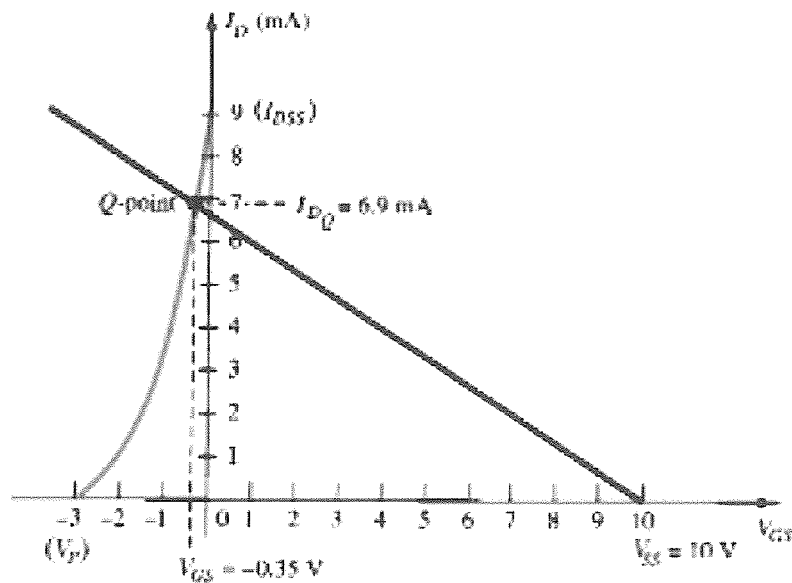


Figure 8 Determining the Q -point for the network of Fig 7a

The transfer characteristics are sketched using the plot point established by $V_{GS} = V_P/2 = -3 \text{ V}/2 = -1.5 \text{ V}$ and $I_D = I_{DSS}/4 = 9 \text{ mA}/4 = 2.25 \text{ mA}$, as also appearing on Fig.8. The resulting operating point establishes the following quiescent levels:

$$I_{DQ} = 6.9 \text{ mA}$$

$$V_{GSQ} = -0.35 \text{ V}$$

(b) Applying Kirchhoff's voltage law to the output side of Fig. 7a will result in

$$-V_{SS} + I_S R_S + V_{DS} + I_D R_D - V_{DD} = 0$$

Substituting $I_S = I_D$ and rearranging gives

$$V_{DS} = V_{DD} + V_{SS} - I_D(R_D + R_S)$$

which for this example results in

$$\begin{aligned} V_{DS} &= 20 \text{ V} + 10 \text{ V} - (6.9 \text{ mA})(1.8 \text{ k}\Omega + 1.5 \text{ k}\Omega) \\ &= 30 \text{ V} - 22.77 \text{ V} \\ &= 7.23 \text{ V} \end{aligned}$$

$$\begin{aligned} \text{(c) } V_D &= V_{DD} - I_D R_D \\ &= 20 \text{ V} - (6.9 \text{ mA})(1.8 \text{ k}\Omega) = 20 \text{ V} - 12.42 \text{ V} \\ &= 7.58 \text{ V} \end{aligned}$$

$$\text{(d) } V_{DS} = V_D - V_S$$

$$\begin{aligned} \text{or } V_S &= V_D - V_{DS} \\ &= 7.58 \text{ V} - 7.23 \text{ V} \\ &= 0.35 \text{ V} \end{aligned}$$